

Introduction to Electronics



An introduction to electronic components and a study of circuits containing such devices.

Week 4: Diodes Part 1





Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Introduction to Electronics

*An introduction to electronic components and a study of circuits
containing such devices.*





Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering



Introduction To PN Junctions

Introduce PN junctions and explain their physical behavior.





Lesson Objectives

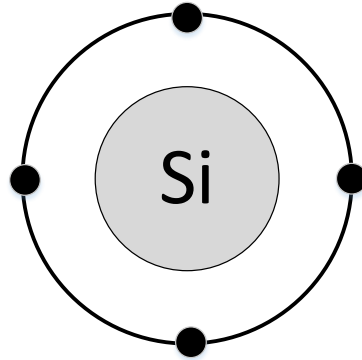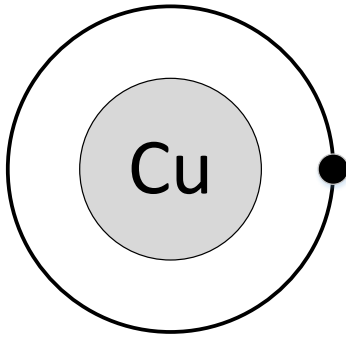- Demonstrate the physics of semiconductors
- Introduce PN Junctions



Semiconductor

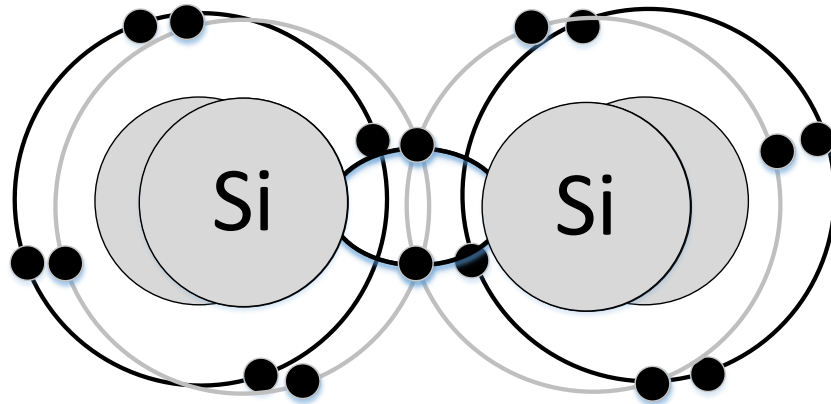

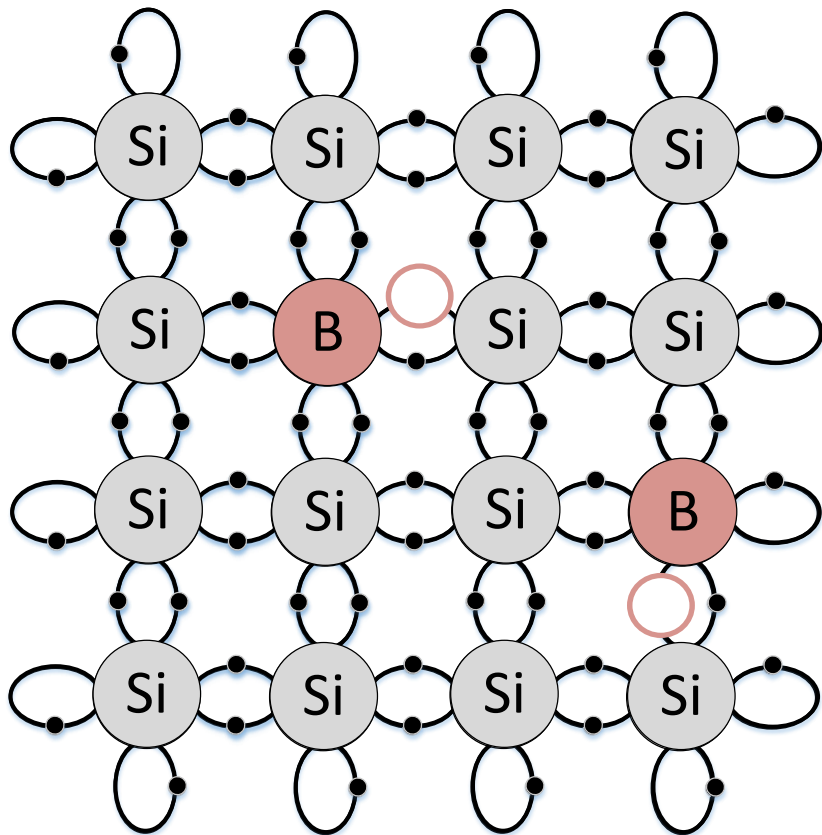


Doping - Add impurities such as Boron or Phosphorus


Number of electrons in outer shell:

- Boron has 3 electrons
- Phosphorus has 5 electrons

P-Type and N-Type Semiconductors

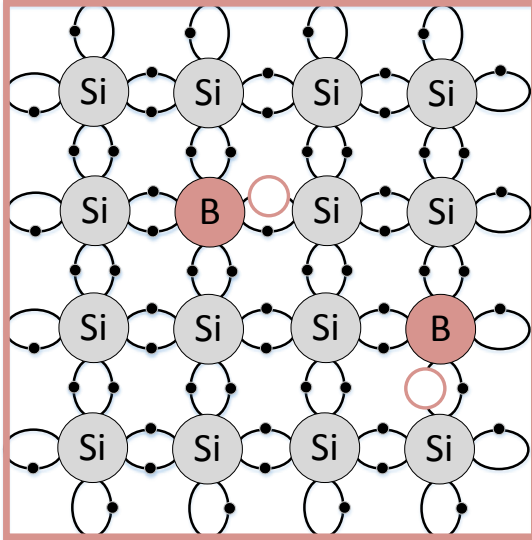


P-Type: extra holes

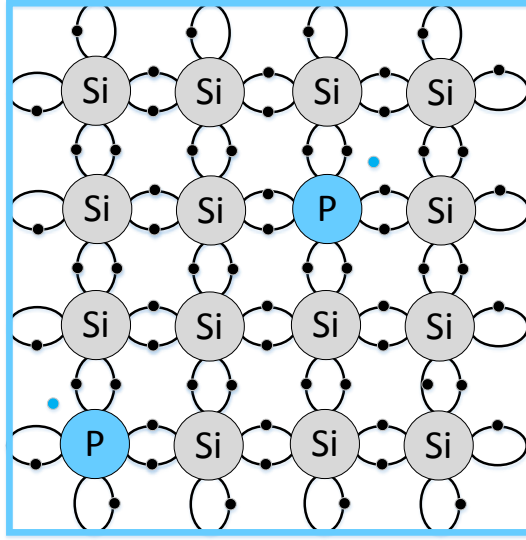

N-Type: extra free electrons

PN Junction

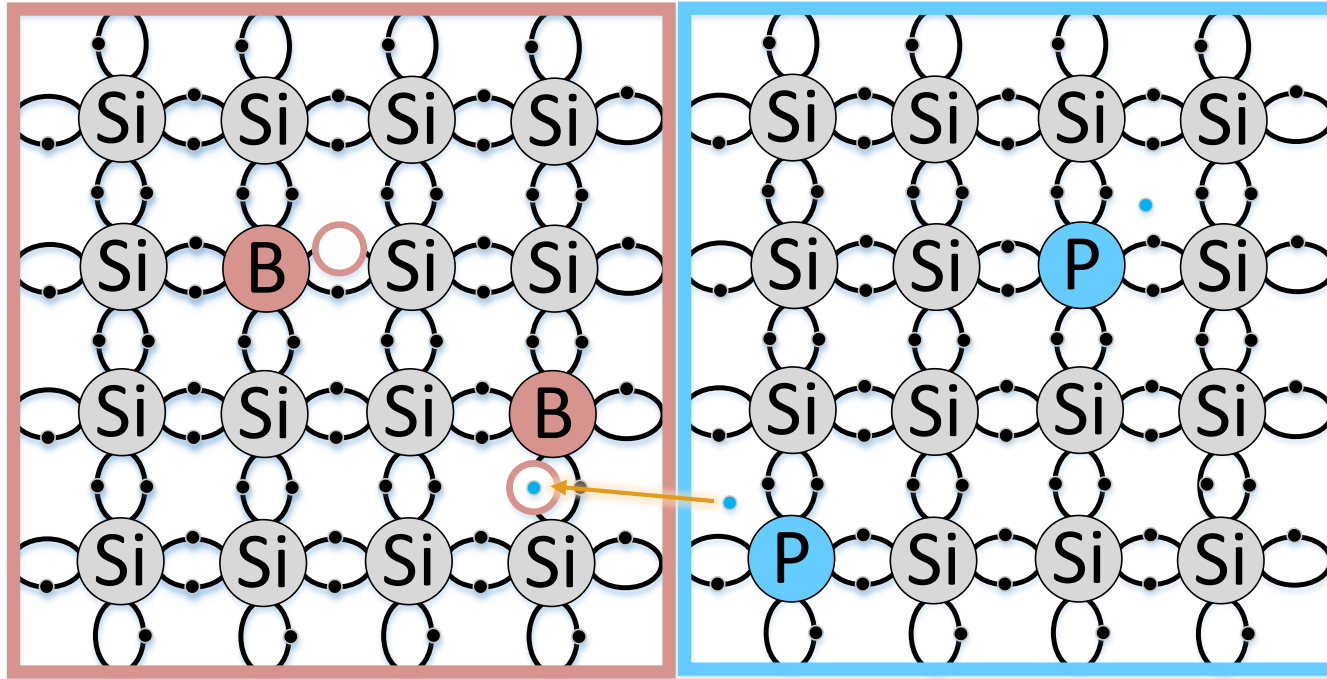


P-Type

N-Type


Energy – heat or light
makes electrons at
the junction diffuse
to fill nearest holes

PN Junction

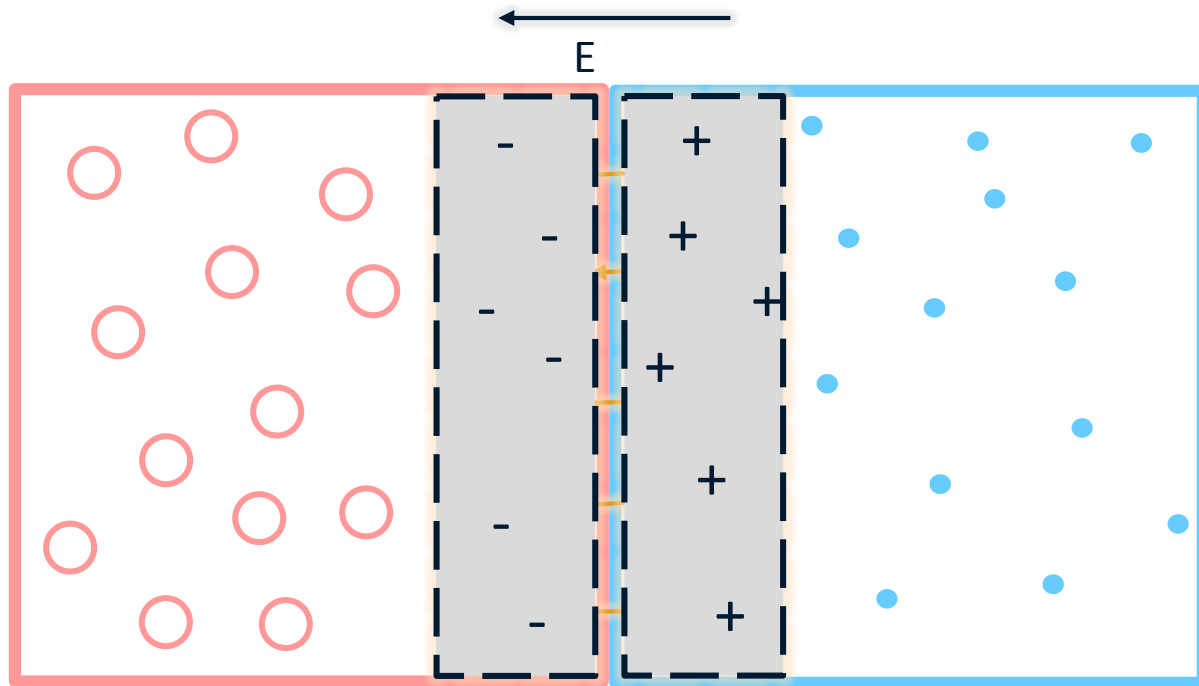


Depletion Region


PN Junction: Conducting

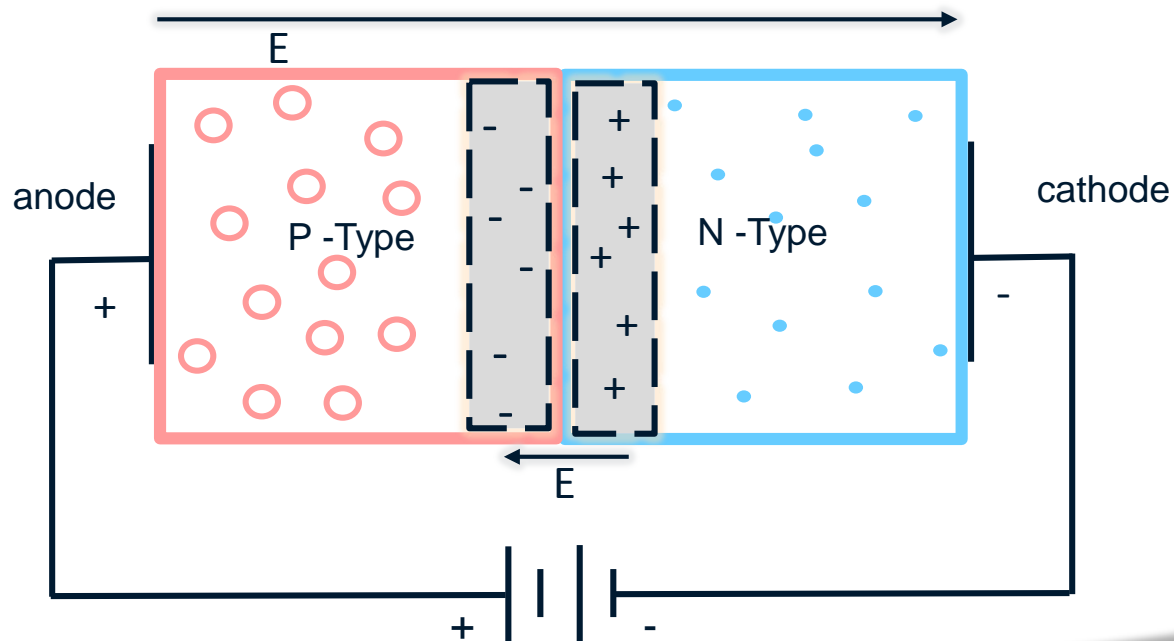

PN Junction: Conducting

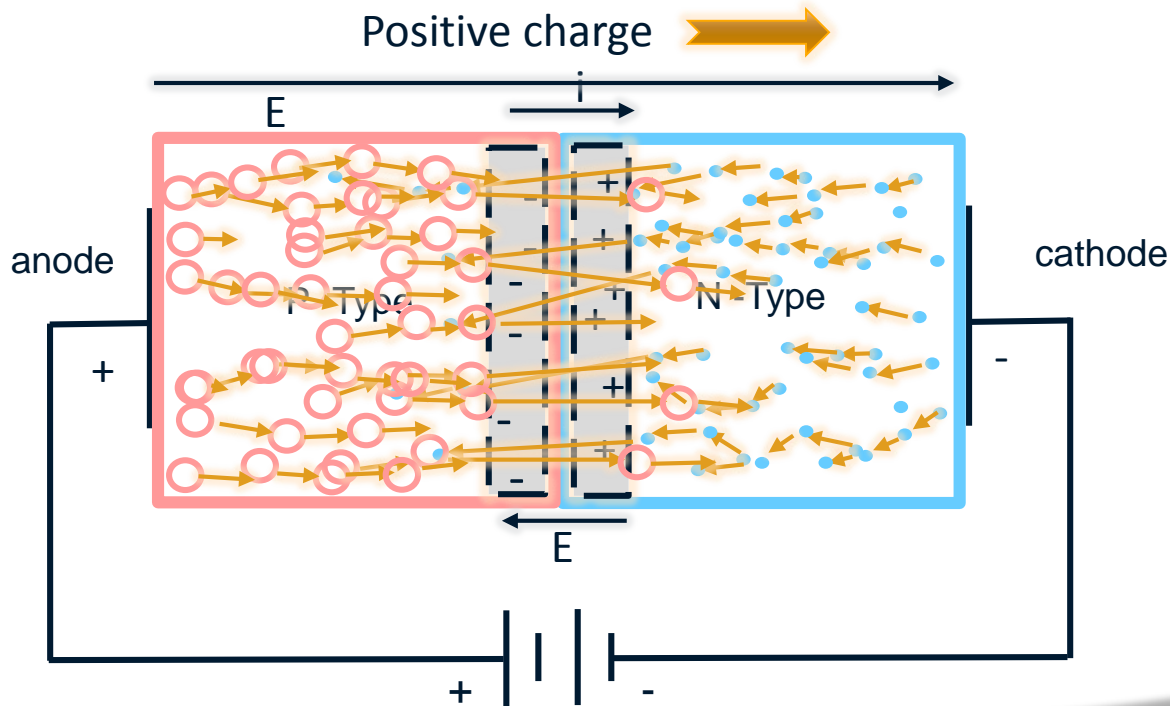


PN Junction: Not Conducting

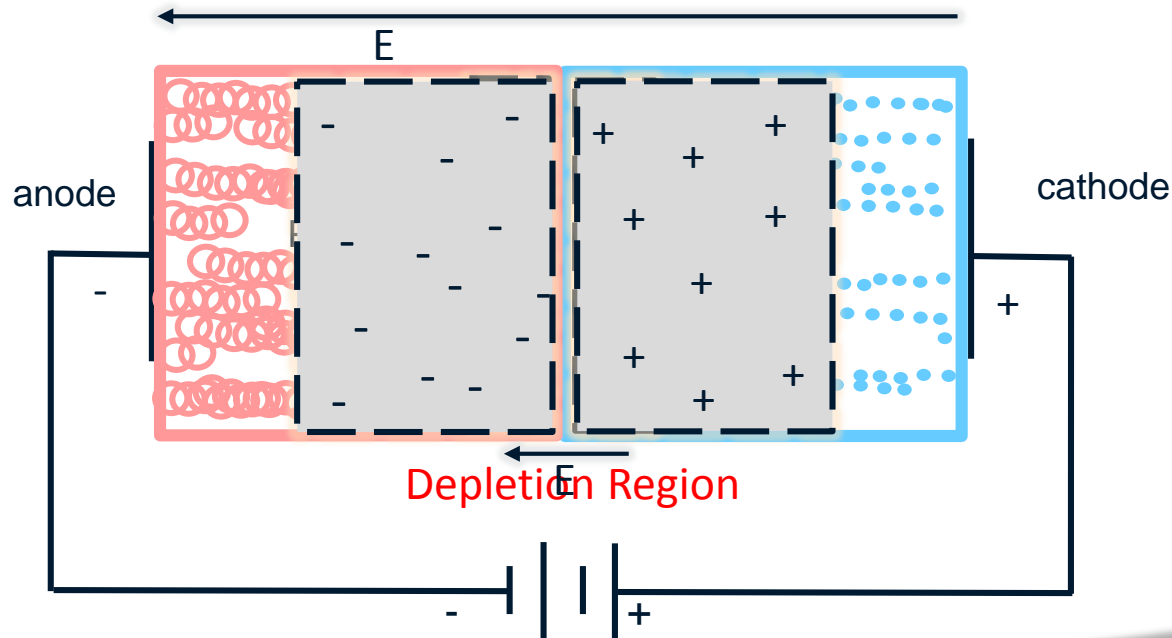


Summary of Behavior



Conducting

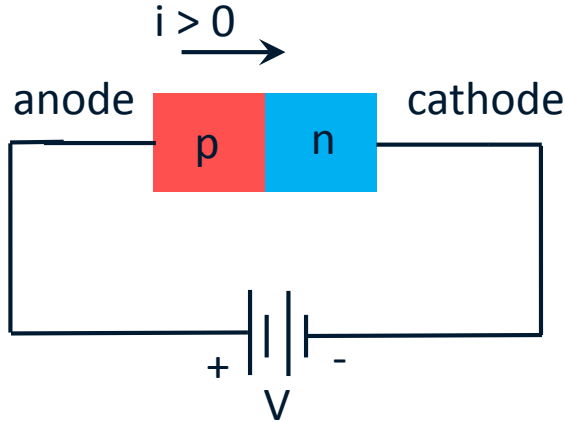

Not Conducting


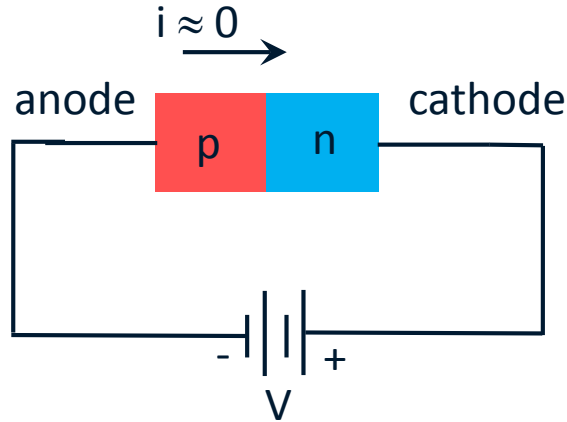


Diode

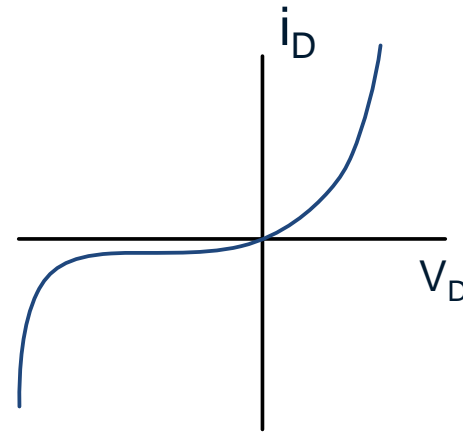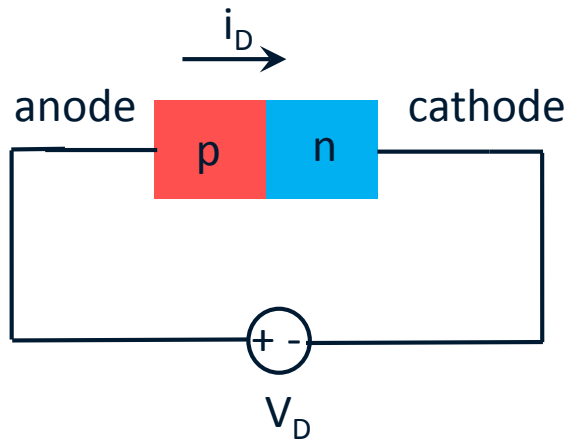

Summary

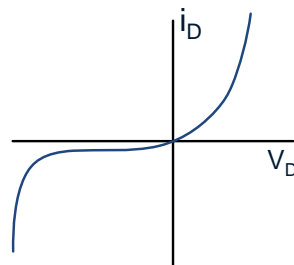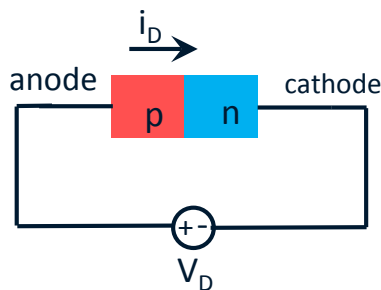- Semiconductors become better conductors when
 - Doped
 - Exposed to heat or light
- PN Junctions (Diodes)



Remainder of Module 3: Diodes

- Circuit analysis with simple diode models
- Applications: rectifiers, AM detector, LEDs, voltage limiters, voltage regulators, AC to DC conversion



Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Diode Behavior and Models

Introduce ideal and non-ideal diode I-V curves




Previous Lesson

- The physics of PN junctions


Lesson Objectives

- ⦿ Analyze diode behavior
- ⦿ Introduce diode applications
- ⦿ Describe different operating regions
- ⦿ Introduce simple diode models that approximate the actual device

Background

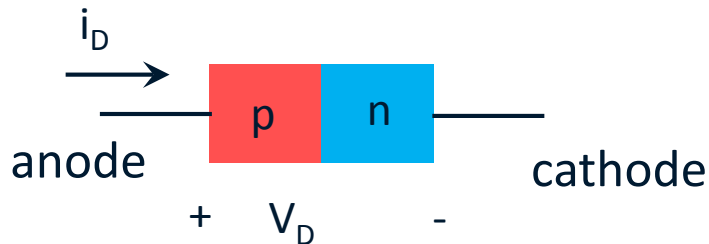




Circuit Symbol:

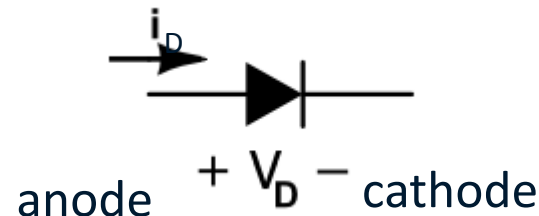


Uses:

- **Block current flow** in a specific direction
- **Rectifier** (AC to DC conversion)
- **Voltage regulator** and **limiter** (protection)
- **Light Emitting Diodes** (LEDs)
- **AM Detectors**
- **Electronic tuners**
- **Photodiodes**


I-V Characteristics

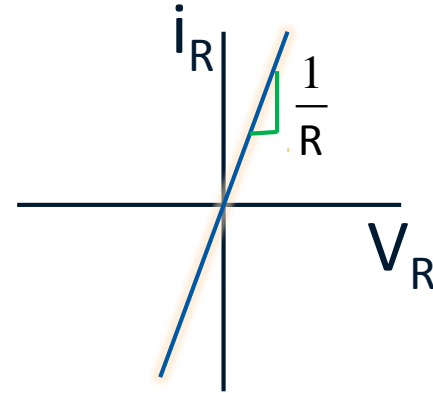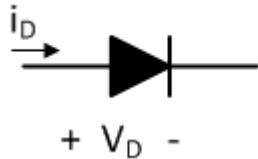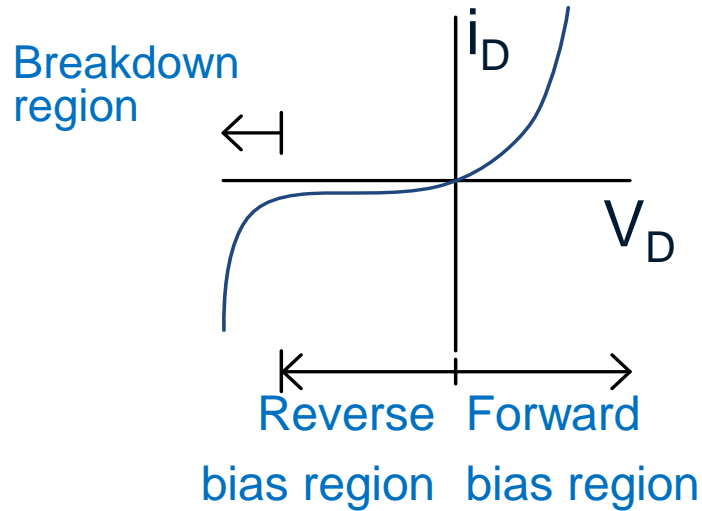


Simple Diode Models

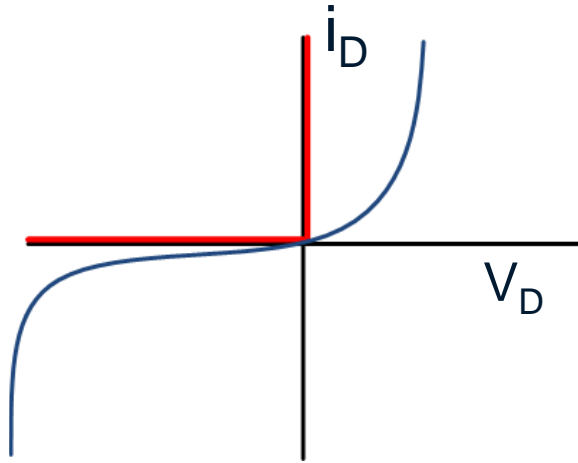

Ideal Diode Model


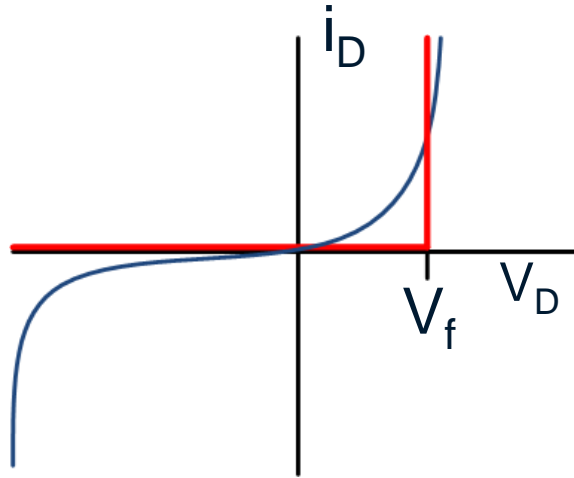


**Ideal Diode + Voltage
Source Model**

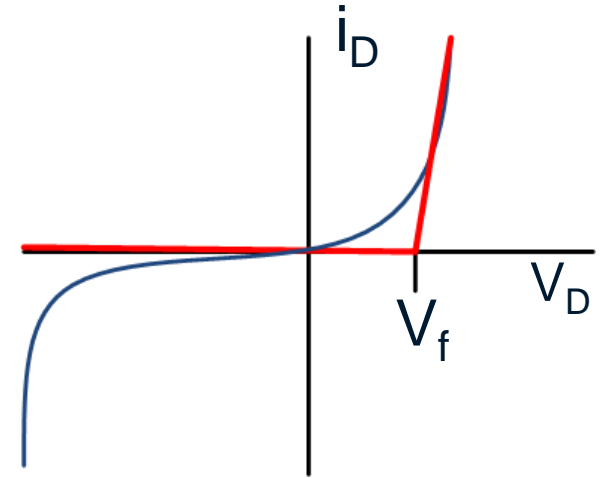

**Ideal Diode + Voltage
Source + Resistor Model**

Ideal Diode

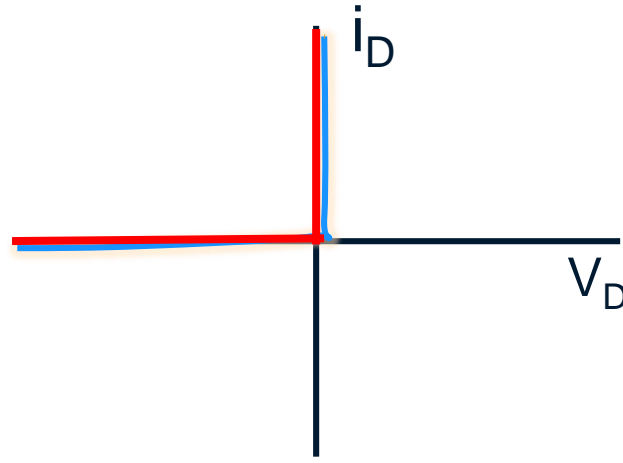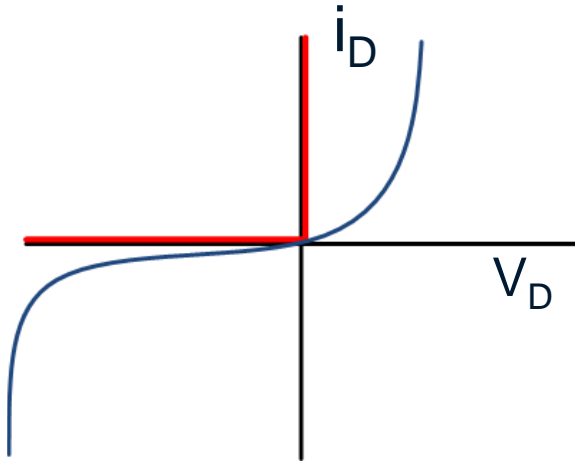

Summary

- Diodes have three operating regions
 - Forward bias, $i_D > 0$
 - Reverse bias, $V_D < 0$
 - Breakdown
- Ideal diodes only allow current to flow in one direction
- Three models: ideal, ideal + voltage source, ideal + voltage source + resistor

Ideal Diode Model



Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering



Introduce ideal diodes in circuits




Lesson Objectives

- Introduce ideal diode operation
- Describe how to analyze DC diode circuits


Ideal Diode Model

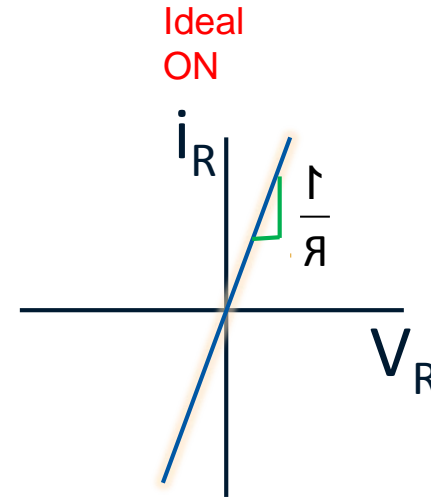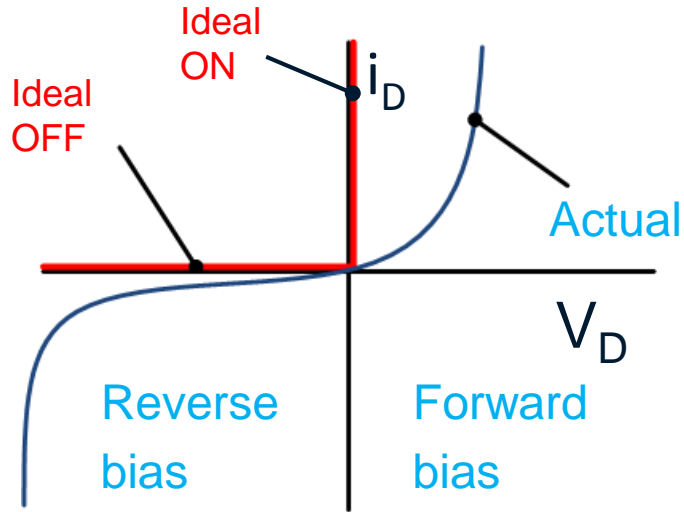



Ideal Diode Model

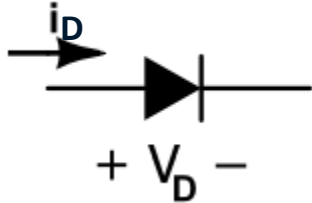

Two possible states: ON and OFF

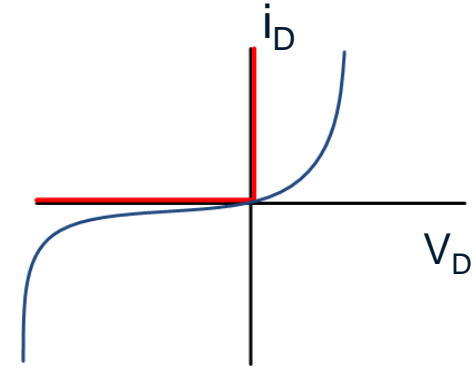


ON (conducting): if $i_D > 0$

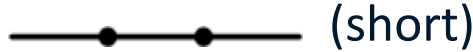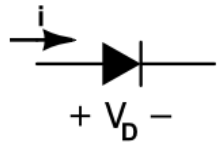



(short)

OFF (blocking): if $V_D < 0$, $i_D = 0$

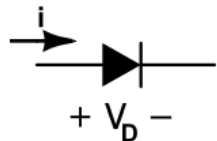

(open)

Example

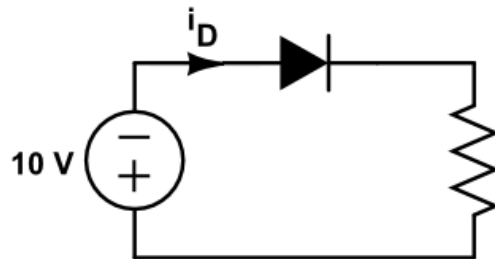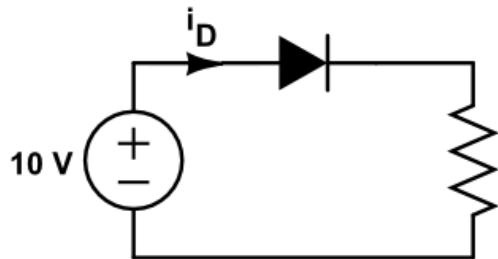

Summary

- Diodes act as a short or an open, depending on the bias



Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Assumed States Method

Introduce ideal diode circuits with multiple diodes






Lesson Objective

- Describe the procedure for handling multiple diodes in a single circuit

Assumed States Procedure

- 1) Identify all possible diode state combinations
 - 1 diode \Rightarrow 2 states
 - 2 diodes \Rightarrow 4 states
 - 3 diodes $\Rightarrow 2^3 = 8$ states
- 2) Analyze each state by replacing the diodes with the corresponding open or short.
- 3) Determine which state is consistent:
 - ON: $i_D > 0$
 - OFF: $V_D < 0$

Example

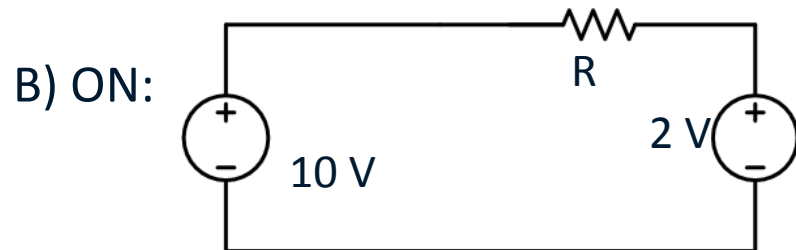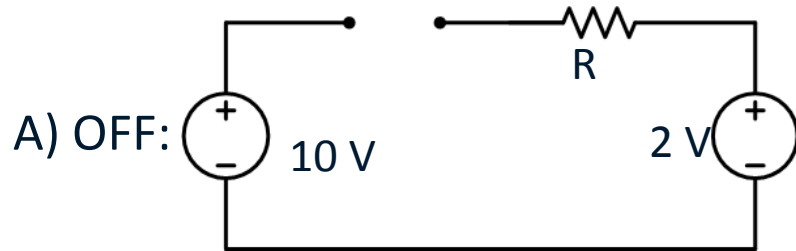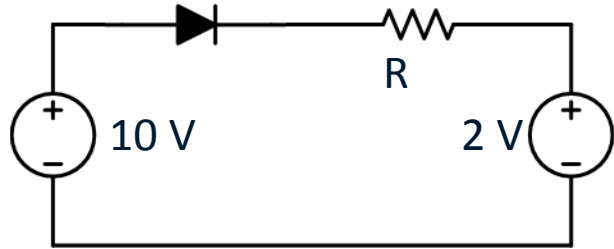

States	D1	Consistent?
A	OFF	
B	ON	


$$-10 + V_D + 2 = 0, V_D > 0$$

(not consistent)

$$-10 + i_D 1k + 2 = 0, i_D = 0.008A > 0$$


(consistent)

Two Diode Example

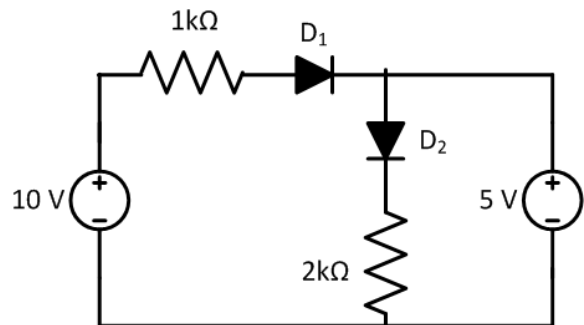


Find V_1

States	D1	D2	Consistent?
A	OFF	OFF	
B	OFF	ON	
C	ON	OFF	
D	ON	ON	

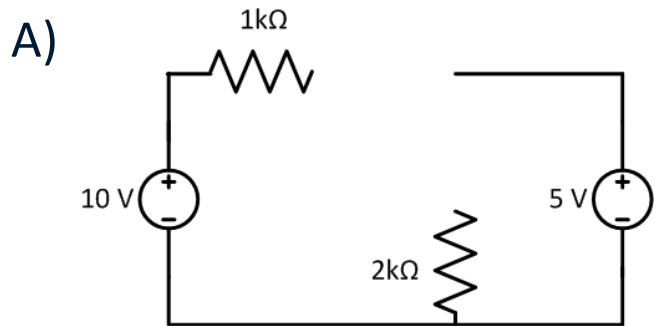


KVL: $-5 + V_{D2} = 0 \Rightarrow V_{D1} = 5 > 0$
(Not consistent)


Example continued

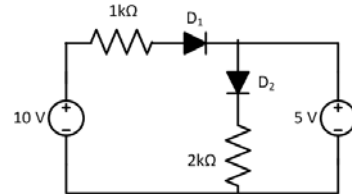

States	D1	D2	Consistent?
A	OFF	OFF	No
B	OFF	ON	
C	ON	OFF	
D	ON	ON	

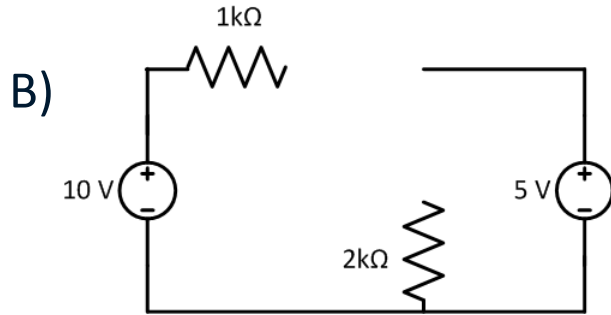


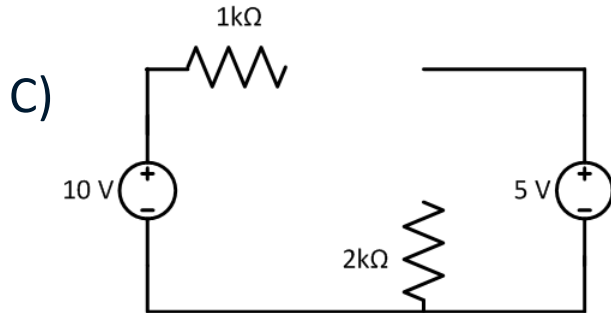KVL: $-10 + V_{D1} + 5 = 0$, $V_{D1} = 5V > 0$
(Not consistent)



$V_{D2} = 5V > 0$
(Not consistent)

Example continued

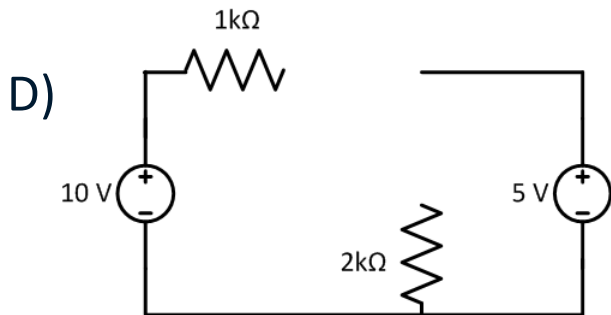


$$\text{KVL: } -10 + 1000i_{D1} + 5 = 0$$

$$i_{D1} = 0.005\text{A} > 0$$

$$i_{D2} = 5/2000 > 0$$

(Consistent)

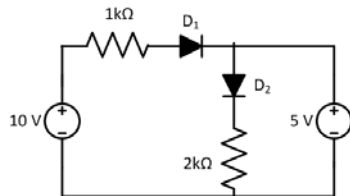

States	D1	D2	Consistent?
A	OFF	OFF	No
B	OFF	ON	No
C	ON	OFF	No
D	ON	ON	

Operating state:

D_1 and D_2 are ON

$$V_1 = 1000(0.005) = 5\text{V}$$

Summary

- Diodes act as a short or an open, depending on the bias
- When solving a circuit, assume each possible state, and check to see if the behavior is consistent with that state



Dr. Bonnie H. Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Ideal Diode + Voltage Source Model


Introduce another diode model for circuit analysis



Lesson Objective

- Examine the ideal diode + voltage source model


Ideal Diode with a Voltage Source

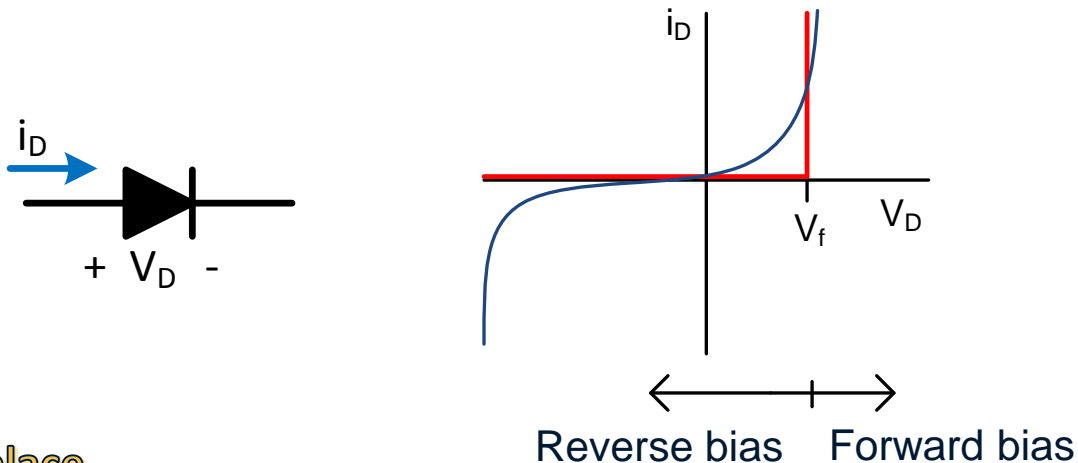

Replace





Example

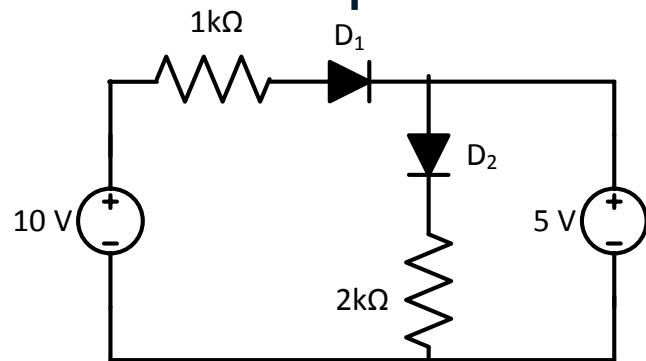

States	D1	D2	Consistent?
A	OFF	OFF	
B	OFF	ON	
C	ON	OFF	
D	ON	ON	

Example

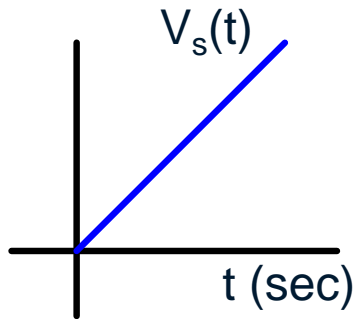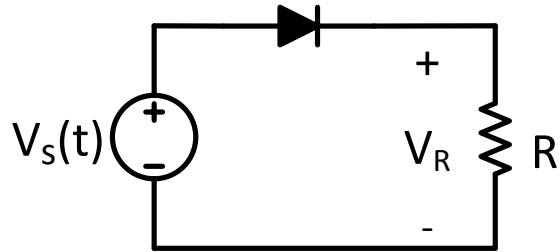

Summary

- Ideal diode + voltage source model has threshold voltage that must be surpassed before the diode is turned on.
 - 0.7 V Silicon
 - 0.3-0.4 V Germanium
 - 1- 4 V LED
- Replace diode with ideal diode + voltage source and analyze using ideal diode methods.