

Introduction to Electronics



An introduction to electronic components and a study of circuits containing such devices.

Week 6: MOSFETs





Introduction and MOSFET Physics

Dr. Bonnie Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Study the physics of MOSFETs



Lesson Objective

- Introduce the uses of transistors
- Investigate the physics of MOSFETs


Types of Transistors

- MOSFET (metal-oxide-semiconductor silicon field-effect transistor)
- BJT (bipolar junction transistor)


Uses of Transistors

- ⦿ Electrically controlled switch (digital circuits/computers)
- ⦿ Amplifier (op amps)
- ⦿ Resistor with value electrically controlled


NMOS (N-type MOSFET)

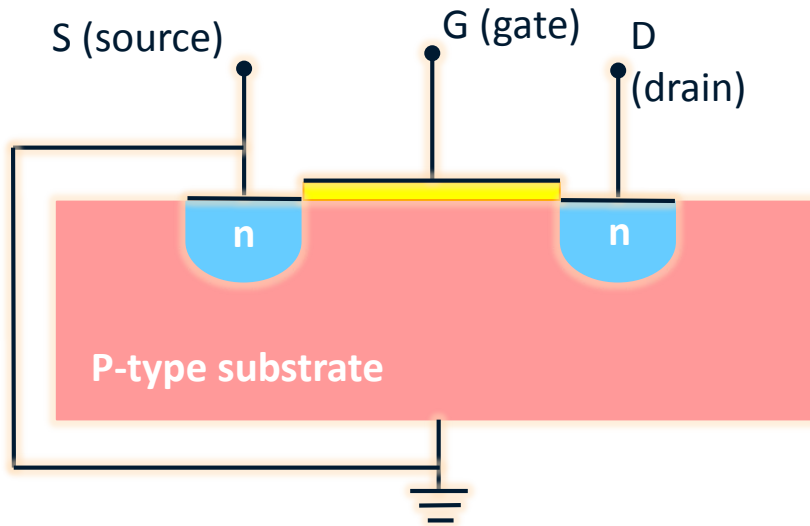



NMOS: Vary V_G

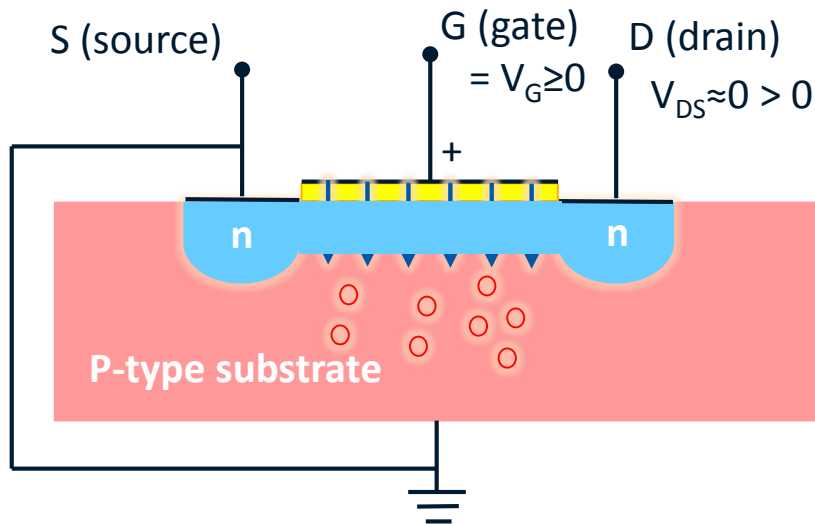


V_{DS} small and constant

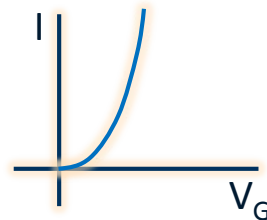

NMOS: Vary V_{DS}

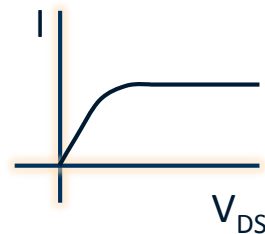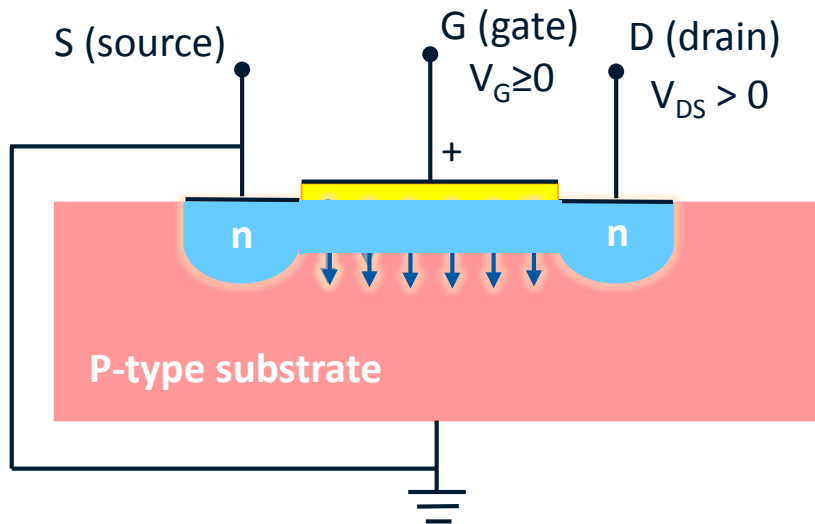

Summary

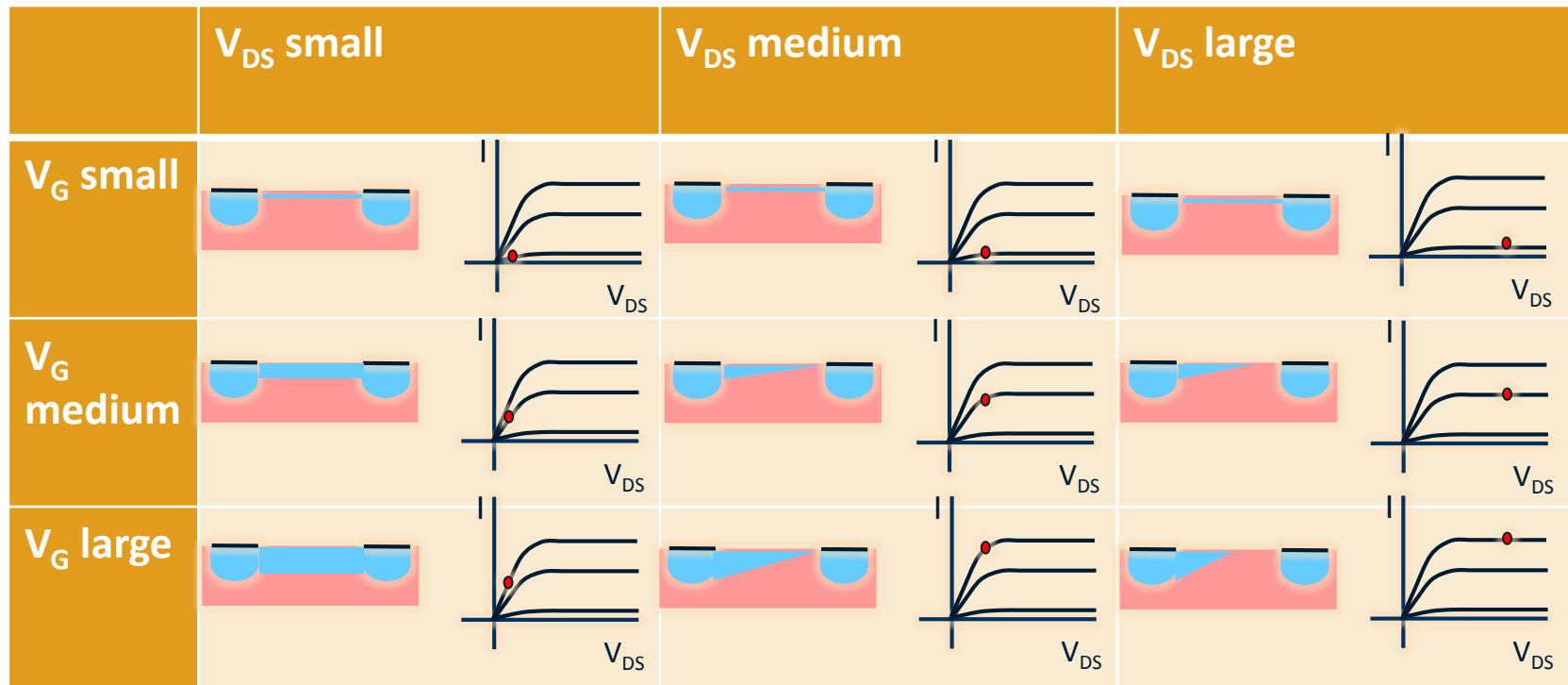

Remainder of Module

- ⦿ MOSFET switches
- ⦿ MOSFET amplifiers
- ⦿ BJTs

MOSFET Switches



Dr. Bonnie Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Introduce the use of MOSFETs as switches in circuits




Previous Lesson

- Introduction to MOSFETs
- The physics of MOSFETs


Lesson Objectives

- Examine the use of MOSFET as a switch in a circuit
- Introduce CMOS devices


NMOS Switch Behavior

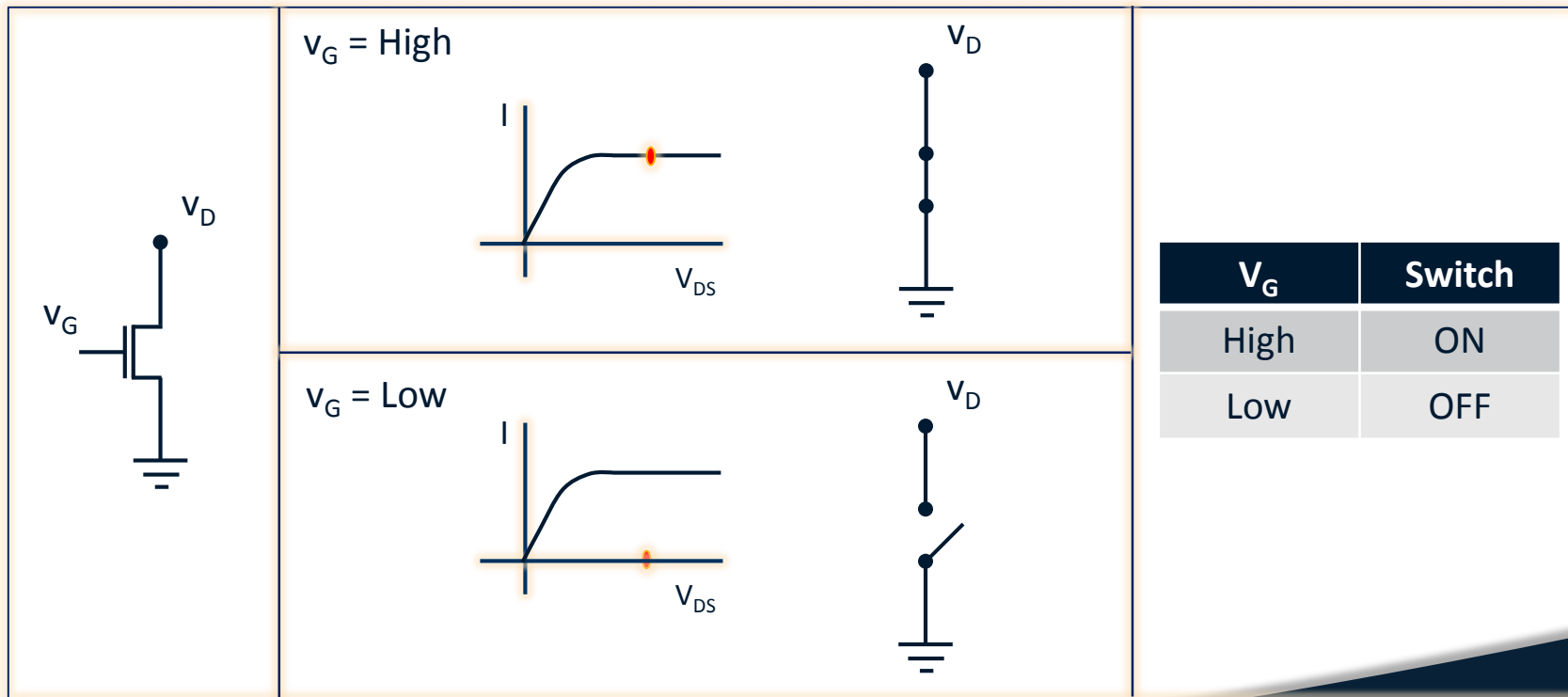

Simple NMOS Inverter Circuit

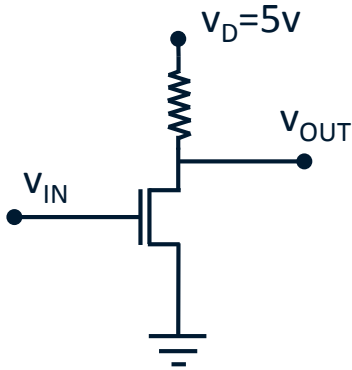

CMOS Devices

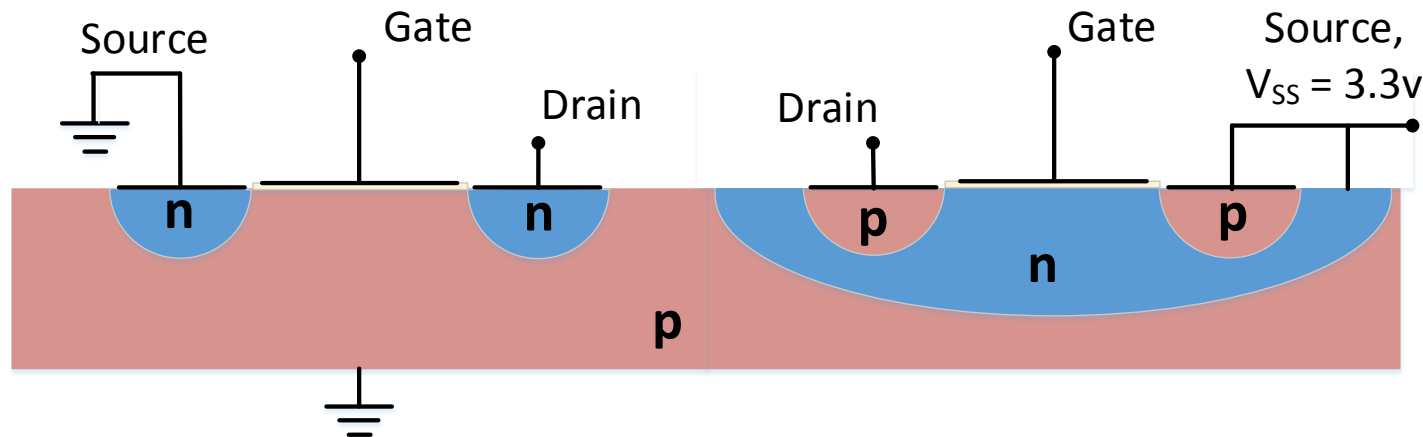

NMOS:


V_G	Switch
High	ON
Low	OFF

PMOS:

V_G	Switch
High	OFF
Low	ON


Summary of Switch Behavior

NMOS

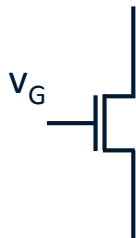


V_G	Switch
High	ON
Low	OFF

PMOS

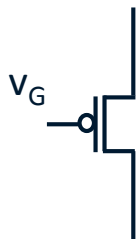

V_G	Switch
High	OFF
Low	ON

CMOS Inverter Circuit

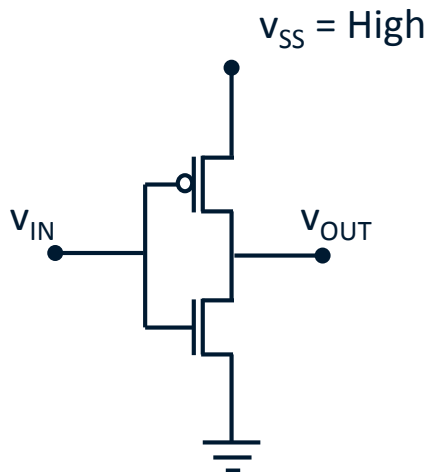

V_{IN}	V_{OUT}
High	Low
Low	High

Summary

- Examine the use of MOSFET as an electrically controlled switch in a circuit
- Introduced CMOS for complementary p-type and n-type transistor behavior
- Introduced inverter circuits

CMOS Logic Gates



Dr. Bonnie Ferri

Professor and Associate Chair
School of Electrical and
Computer Engineering

Introduction to logic gates made from CMOS transistors






Previous Lesson

○ MOSFET Switches

Lesson Objectives

- Introduce logic gates and their transistor circuits
 - NOT, NAND, NOR, AND, OR

CMOS NOT Gate (Inverter Circuit)

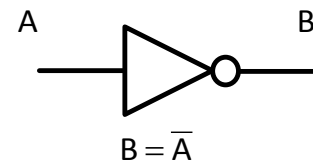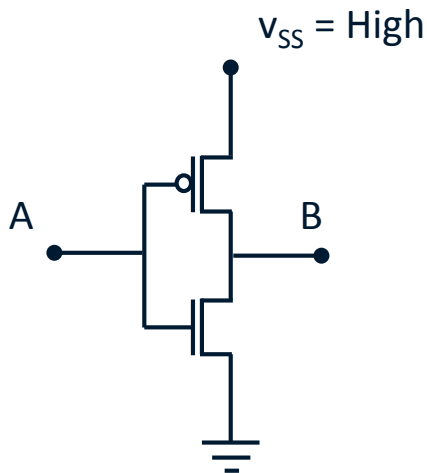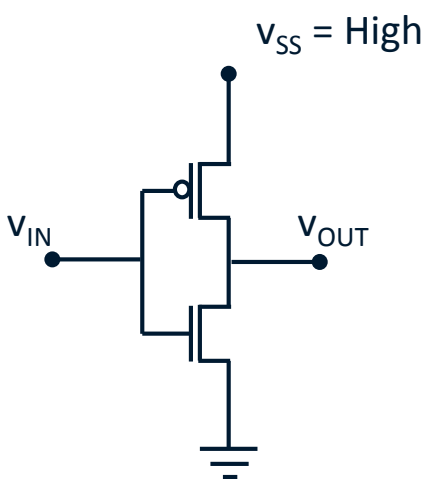

Truth Table


V_{IN}	V_{OUT}
High	Low
Low	High

A	B
0	1
1	0

Logic Gates


NOT

A	B
0	1
1	0

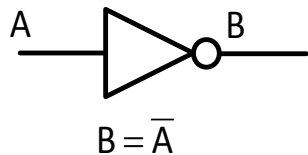


AND

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

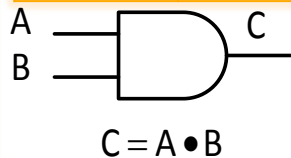


NAND

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

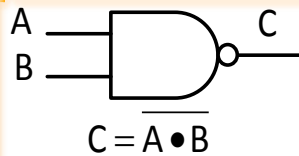


OR

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

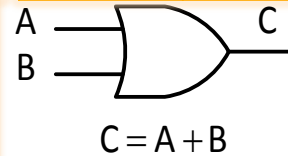


NOR

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

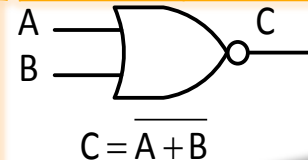


PMOS Switch Behavior

NMOS

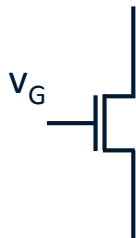

V_G	Switch
High	ON
Low	OFF

PMOS



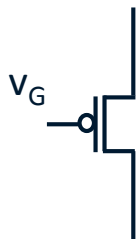


V_G	Switch
High	OFF
Low	ON

NAND Gate

NAND




A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

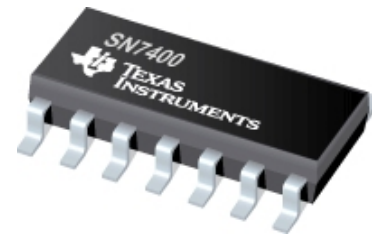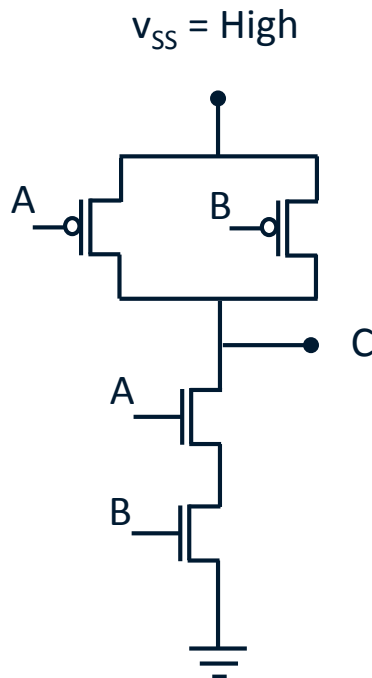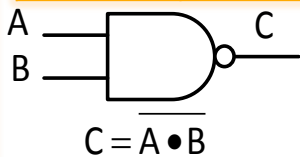

NOR Gate

NOR

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

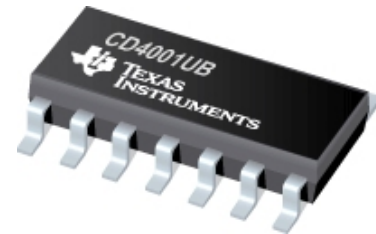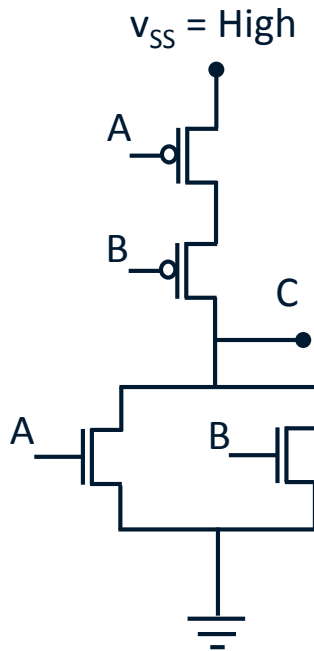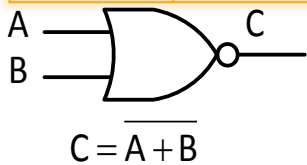

Summary


- Logic gate circuits are made from CMOS n-type and p-type transistors



Dr. Allen Robinson

Academic Professional
School of Electrical and
Computer Engineering

Introduction to Electronics



*An introduction to electronic components and a study of circuits
containing such devices.*



Dr. Allen Robinson

Academic Professional
School of Electrical and
Computer Engineering

MOSFET Characteristics

Introduce MOSFET characteristic curves and biasing



Previous Lesson


- Introduced CMOS logic gates

Lesson Objectives


- Introduce MOSFET characteristic curves
- Introduce dc biasing

Characteristic Curves

MOSFET Output Characteristics

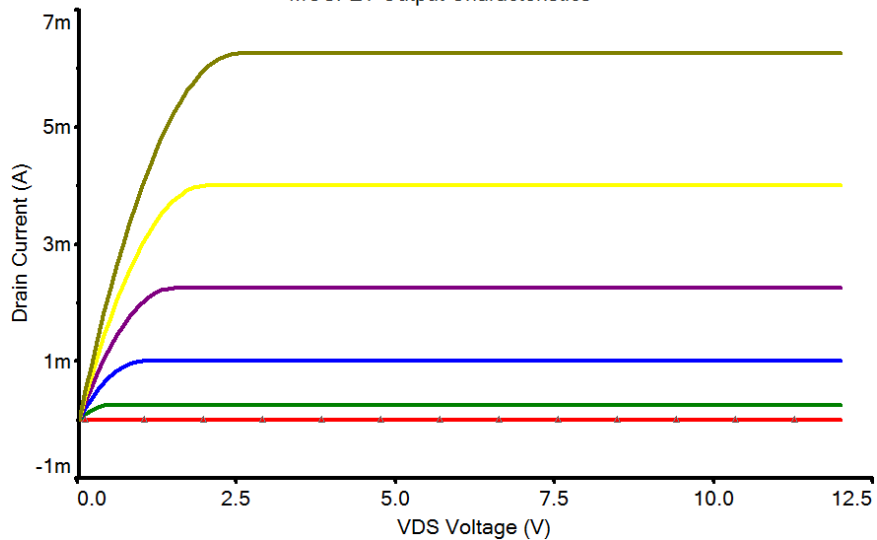


MOSFET Transfer Characteristic

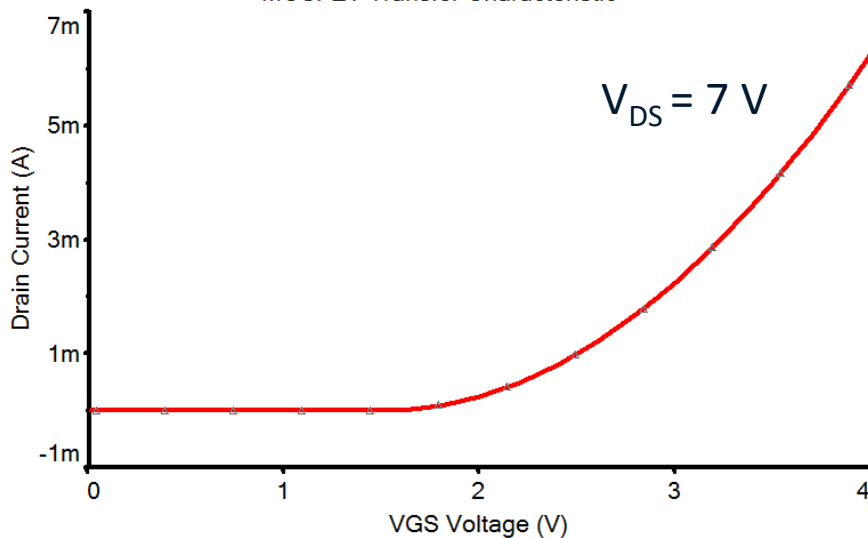

Regions of Operation

MOSFET Output Characteristics

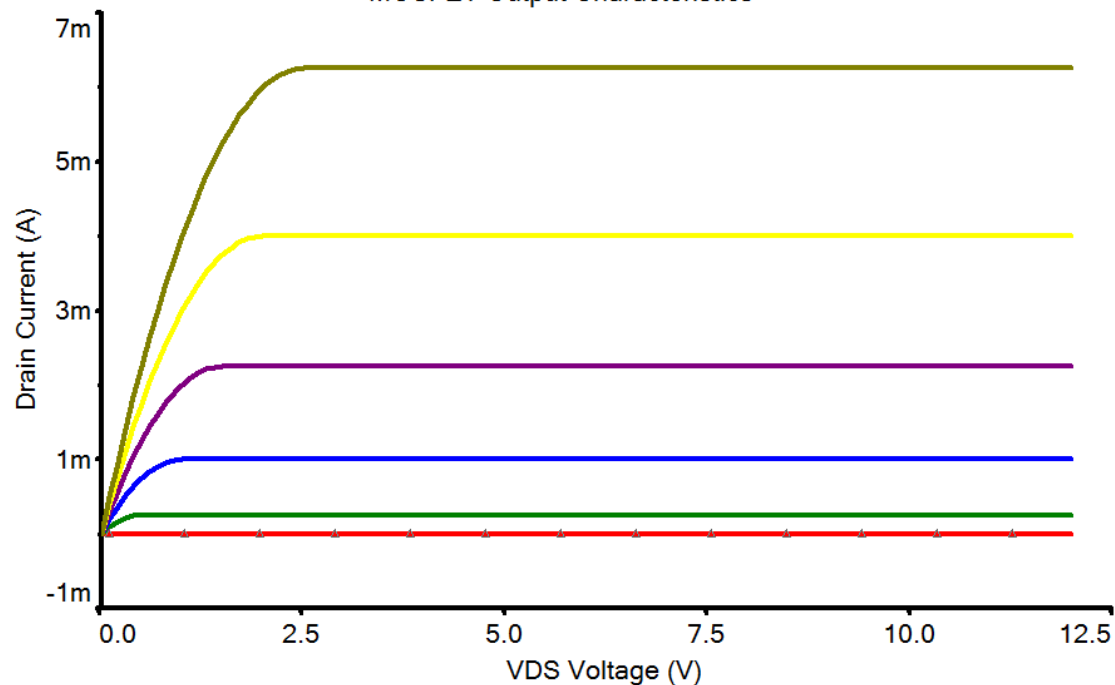

Regions of Operation

Cutoff Region

$$V_{GS} < V_{TO}$$

$$I_D = 0$$

Linear/Triode Region

$$V_{GS} > V_{TO}$$

$$V_{DS} < V_{GS} - V_{TO}$$

$$I_D = 2K \left[(V_{GS} - V_{TO}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Saturation Region

$$V_{GS} > V_{TO}$$


$$V_{DS} > V_{GS} - V_{TO}$$

$$I_D = K(V_{GS} - V_{TO})^2$$

K = Transconductance parameter. Units of A/V^2

V_{TO} = Threshold or turn on voltage. Minimum value of V_{GS} for I_D to flow.

Transfer Characteristics

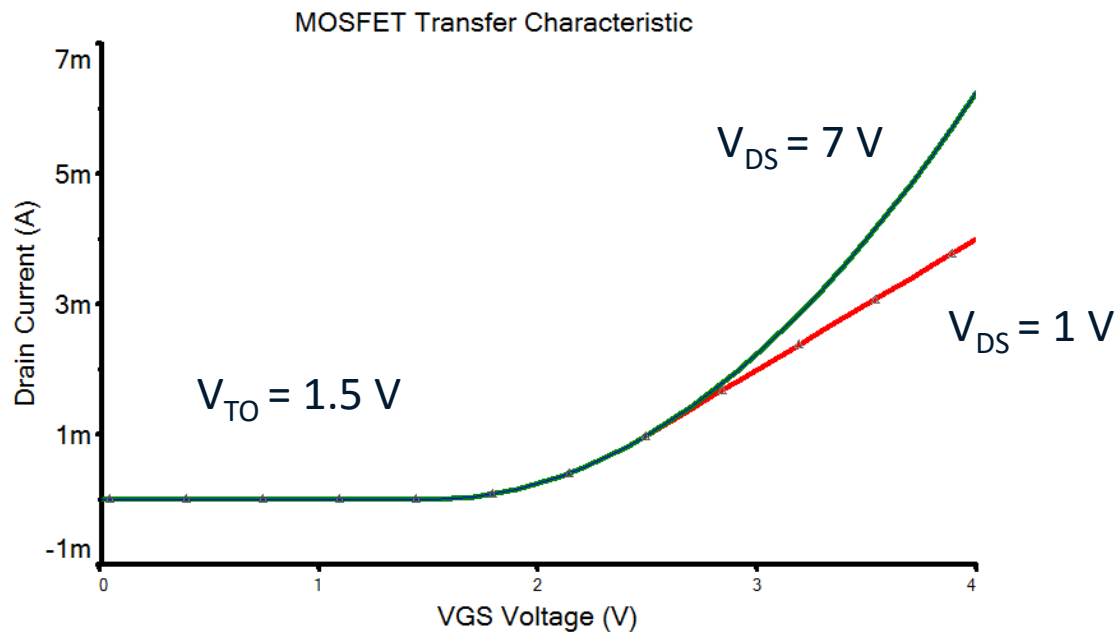

Summary

- Introduced MOSFET characteristics
- Introduced dc biasing

Next Lesson

- Common Source Amplifier: DC Analysis



Dr. Allen Robinson

Academic Professional
School of Electrical and
Computer Engineering

Introduction to Electronics

*An introduction to electronic components and a study of circuits
containing such devices.*





Dr. Allen Robinson
Academic Professional
School of Electrical and
Computer Engineering

Common Source Amplifier: DC Analysis

Introduce common source amplifier



Previous Lesson


- Examined MOSFET characteristic curves and biasing

Lesson Objectives


- Introduce common source amplifier
- Analyze common source amplifier dc circuit

MOSFET Gain Stage

Common Source Amplifier

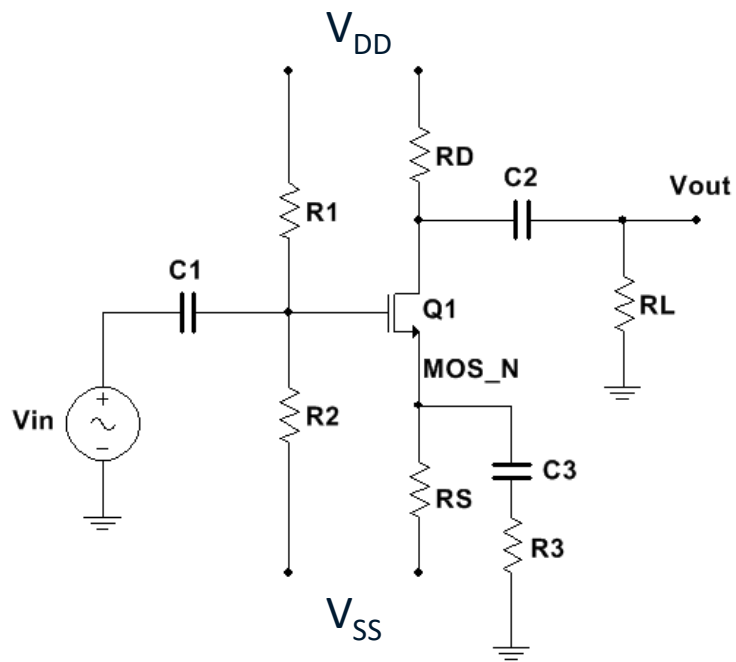


Common Source Amplifier DC Circuit

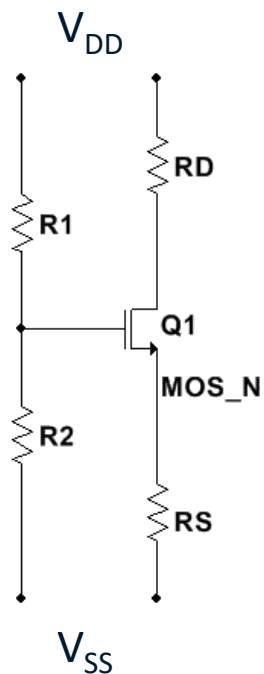

$$I_G = 0$$

$$I_D = I_S$$

Common Source Amplifier DC Formulas

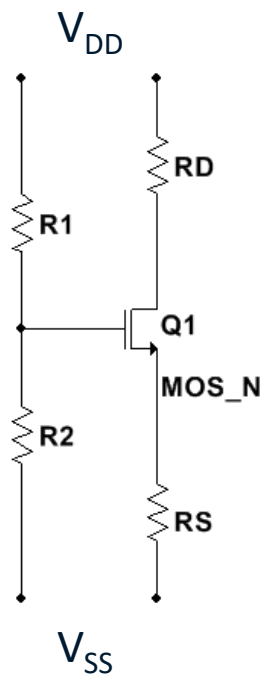

$$I_G = 0$$

$$I_D = I_S$$

$$V_G = \frac{V_{DD}R_2 + V_{SS}R_1}{R_1 + R_2}$$

$$V_{GS} = \sqrt{\frac{I_D}{K}} + V_{TO}$$

$$V_1 = V_G - V_{SS} - V_{TO}$$

$$I_D = \left(\frac{\sqrt{1 + 4KV_1R_S} - 1}{2\sqrt{K}R_S} \right)^2$$

$$V_D = V_{DD} - R_D I_D$$

$$V_S = V_{SS} + R_S I_S$$

Summary

- Introduced common source (CS) amplifier
- Introduced dc analysis of CS amplifier

Next Lesson

- Common Source Amplifier: AC Analysis



Dr. Allen Robinson

Academic Professional
School of Electrical and
Computer Engineering

Introduction to Electronics



*An introduction to electronic components and a study of circuits
containing such devices.*



Dr. Allen Robinson

Academic Professional
School of Electrical and
Computer Engineering

Common Source Amplifier: AC Analysis

Examine ac behavior of the common source amplifier



Previous Lesson

- Introduced common source amplifier
- Introduced dc biasing

Lesson Objectives

- Introduce ac behavior of CS amplifier
- Analyze CS amplifier circuit

Small Signal Parameters and Gain


Perform small-signal analysis to obtain:

$$g_m = 2\sqrt{KI_D} \quad \text{Transconductance}$$


$$r_s = 1/g_m \quad \text{Intrinsic source resistance}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_D || R_L}{r_s + R_S || R_3} \quad \text{Midband Gain}$$

Common Source Amplifier

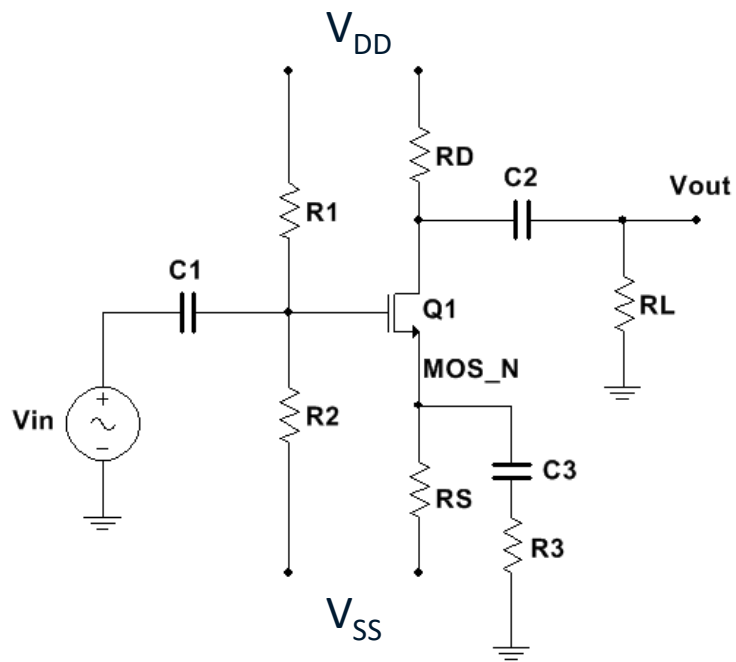


Common Source Amplifier Example

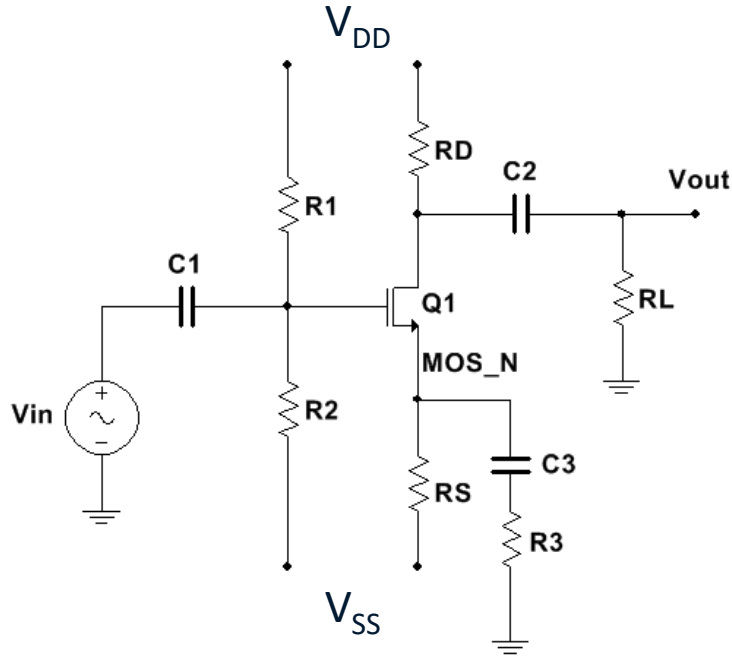

Determine Q point and Gain Given:

$$\begin{aligned}
 R_1 &= 1 \text{ M}\Omega & V_{DD} &= +15 \text{ V} \\
 R_2 &= 200 \text{ k}\Omega & V_{SS} &= -15 \text{ V} \\
 R_S &= 3 \text{ k}\Omega \\
 R_L &= 20 \text{ k}\Omega \\
 R_3 &= 51 \Omega \\
 R_D &= 15 \text{ k}\Omega \\
 K &= 0.001 \text{ A/V}^2 \\
 V_{TO} &= 1.5 \text{ V}
 \end{aligned}$$

Common Source Amplifier Example

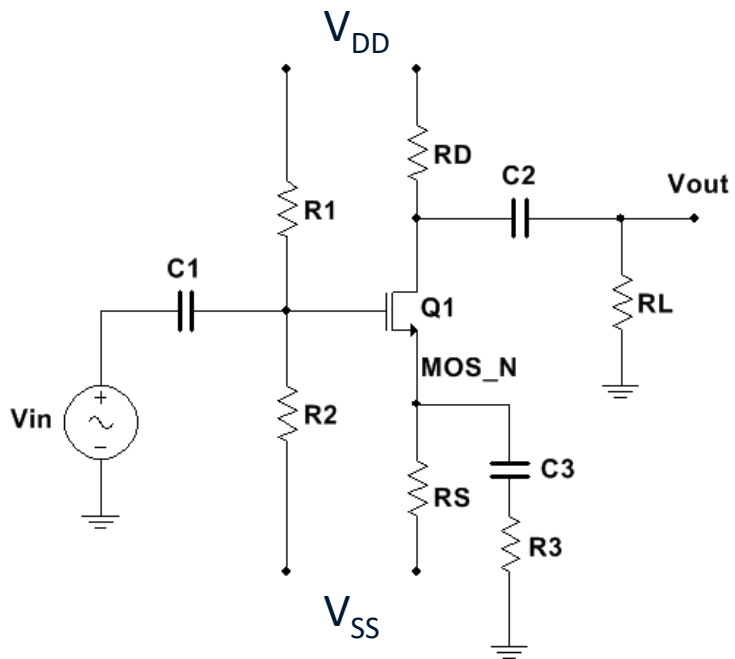

Summary

- Introduced AC analysis of CS amplifier
- Analyzed CS amplifier circuit

Next Lesson

- Bipolar Junction Transistor (BJT)